

# Lecture 38, Apr 11, 2022

## Complex Power

- So far all of the types of power are real numbers; complex power is the only type of power that is complex
- The *complex power* for a sinusoidal AC circuit is defined as  $\mathbf{S} = \frac{1}{2}\mathbf{V}\mathbf{I}^* = \mathbf{V}_{rms}\mathbf{I}_{rms}^*$  where  $\mathbf{V} = V_m\angle\theta_v$ ,  $\mathbf{I} = I_m\angle\theta_i$ 
  - Complex power also has units of volt-amps
- We can also write complex power as  $\mathbf{S} = \frac{1}{2}(V_m\angle\theta_v)(I_m\angle-\theta_i) = \frac{1}{2}V_mI_m\angle(\theta_v - \theta_i)$ 
  - Recall the apparent power  $S = \frac{1}{2}V_mI_m$ , so the complex power has an amplitude equal to the apparent power
- Using Euler's formula, in rectangular form  $\mathbf{S} = V_{rms}I_{rms} \cos(\theta_v - \theta_i) + jV_{rms}I_{rms} \sin(\theta_v - \theta_i)$
- Complex power is related to average/active and reactive power by  $\mathbf{S} = P_{ave} + jQ$
- The power factor is the cosine of the angle of the complex power
- Consider an impedance  $\mathbf{Z} = R + jX$ , complex power is  $\mathbf{S} = \mathbf{V}_{rms}\mathbf{I}_{rms}^*$ 
$$\begin{aligned} &= \mathbf{Z}\mathbf{I}_{rms}\mathbf{I}_{rms}^* \\ &= (R + jX)|\mathbf{I}_{rms}|^2 \\ &= RI_{rms}^2 + jXI_{rms}^2 \\ &= P_{ave} + Q \end{aligned}$$
- $\mathbf{S}$ ,  $P$  and  $Q$  form a triangle in the complex plane
- Conservation of power: the algebraic sum of all the complex powers in a circuit is zero,  $\sum_{k=1}^n \mathbf{S}_k = 0$   
where  $n$  is the number of circuit elements
  - Since complex power has a real and imaginary component, conservation of power holds for both average and reactive power separately